

CLASS - X Physics	Worksheet -1	Electricity
-------------------	--------------	-------------

Numericals

- 1. When a 4V battery is connected across an unknown resistor there is a current of 100 mA in the circuit. The value of the resistance of the resister is:
 - a) 4 Ω
 - b) 40 Ω
 - c) 400 Ω
 - d) 0.4 Ω
- 2. a) Calculate the energy transferred when 2 A current flows through a 10 Ω resistor for 30 minutes.
 - b) Calculate the amount of charge that would flow in one hour through the element of an electric iron drawing a current of 0.4 amps
- 3. Two resistances of 4 Ω and 8 Ω are connected in parallel. What would be the combined resistance of the system?
- 4. Two identical resistors each of resistance 2 Ohm are connected in turn (1) in series (2) in parallel to a battery of 12 V. Calculate the ratio of power consumed in two cases.
- 5. (i) A 100 W electric bulb is connected to 220 V mains power supply. Calculate the strength of the electric current passing through the bulb.
 - (ii) If the same bulb is taken to U.S.A where the main power supply is 110 V, how much electric current will pass through the bulb when connected to mains?
- 6. Calculate the resistance of 2 km long copper wire of radius 2 mm. (Resistivity of copper = 1.72×10^{-8})
- 7. A wire of length 3 m and area of cross-section 1.7×10^{-6} m² has a resistance 3×10^{-2} ohm.
 - a. What is the formula for resistivity of the wire and what is the unit of it b. Calculate the resistivity of the wire
- 8. Two electric lamps of 100W and 25W respectively are connected in parallel to a supply voltage of 200V. Calculate the total current flowing through the circuit.
- 9. A cylindrical conductor of length 1 and uniform area of cross section A has resistance R. Another conductor of the same material and resistance R has length 21. What will be its area of cross section?
- 10. A current of 5A passes through a 20hm resistor for 30 minutes. Calculate the electrical energy transferred.